

Single Cycle RV_RISC-V Data_path Architecture


NCDC



Complete Architecture

The datapath follows the same general stage of computation:

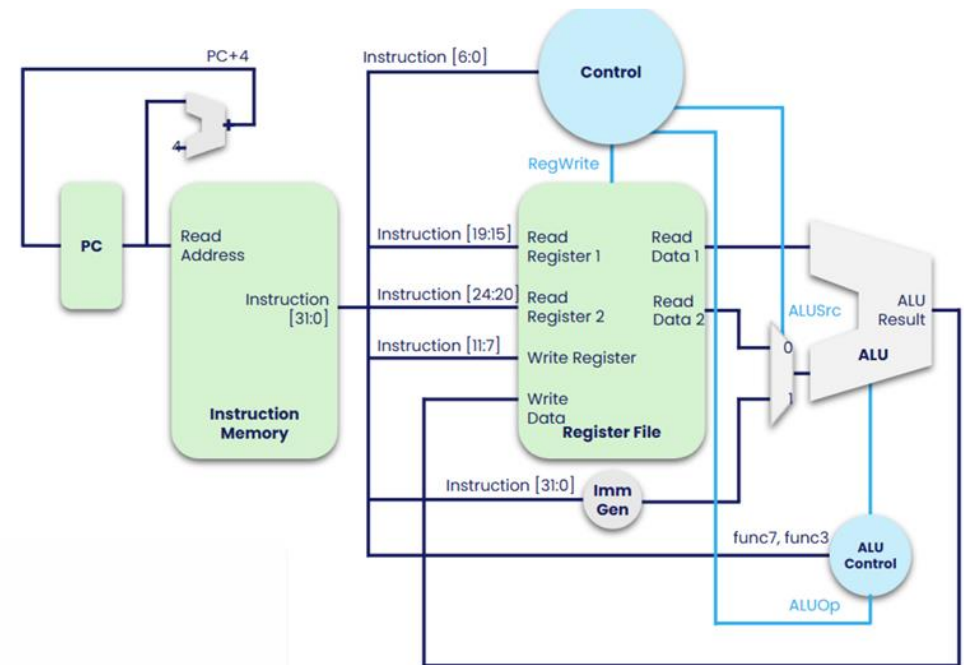1. **Instruction Fetch (IF)**
2. **Instruction Decode (ID)**
3. **Execute (EX)**
4. **Memory (MEM)**
5. **Write Back (WB)**





3 Program counter

```

module PC #(parameter size = 1024 ) (
input logic clk,
input logic reset,
output logic [$clog2(size*4)-1 :0]count
);

    always_ff @(posedge clk)
    begin
        if(reset) begin count <= '0; end
        else if(count == (size*4 - 4) )begin
            count<= '0;
            end
        else begin
            count <= count + 4; end
        end
    endmodule

```

  

Instruction Memory

```

module Instruction_memory #(parameter I_memDepth = 1024) (
    input logic [31:0]counter,
    output logic [31:0]instruction
);


    localparam MemDepth = $clog2(I_memDepth);
    logic [31: 0]I_mem[0: MemDepth - 1];


    initial begin
        $readmemh("I_mem.mem", I_mem);
    end

    assign instruction = I_mem[counter[31:2]];

endmodule

```

 

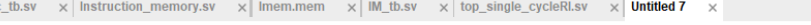

Instruction Tables:

I-Type Instructions

These instructions have one immediate operand which is specified in the instruction encoding as can be seen from the encoding below

imm[11:0]	rs1	funct3	rd	opcode
-----------	-----	--------	----	--------

A list of immediate instructions is shown in table below

op	funct3	funct7	Type	Instruction	Description	Operation
0010011 (19)	000	-	I	addi rd, rs1, imm	add immediate	rd = rs1 + SignExt(imm)
0010011 (19)	001	0000000*	I	slli rd, rs1, uimm	shift left logical immediate	rd = rs1 << uimm
0010011 (19)	010	-	I	slti rd, rs1, imm	set less than immediate	rd = (rs1 < SignExt(imm))
0010011 (19)	011	-	I	sltiu rd, rs1, imm	set less than imm. unsigned	rd = (rs1 < SignExt(imm))
0010011 (19)	100	-	I	xori rd, rs1, imm	xor immediate	rd = rs1 ^ SignExt(imm)
0010011 (19)	101	0000000*	I	srlr rd, rs1, uimm	shift right logical immediate	rd = rs1 >> uimm
0010011 (19)	101	0100000*	I	srair rd, rs1, uimm	shift right arithmetic imm.	rd = rs1 >>> uimm
0010011 (19)	110	-	I	ori rd, rs1, imm	or immediate	rd = rs1 SignExt(imm)
0010011 (19)	111	-	I	andi rd, rs1, imm	and immediate	rd = rs1 & SignExt(imm)

Immediate Generation Unit

31 30 29 28 27 26 25 24 23 22 21 20 19 18 17 16 15 14 13 12 11 10 09 08 07 06 05 04 03 02 01 00

R-Type Instructions

The R-Type Instructions have the following encoding

31	25	24	20	19	15	14	12	11	7	6	0
R	funct7	rs2	rs1	funct3	rd	opcode					

and include the instructions given in the table below

op	funct3	funct7	Type	Instruction	Description	Operation
0110011 (51)	000	0000000	R	add rd, rs1, rs2	add	rd = rs1 + rs2
0110011 (51)	000	0100000	R	sub rd, rs1, rs2	sub	rd = rs1 - rs2
0110011 (51)	001	0000000	R	sll rd, rs1, rs2	shift left logical	rd = rs1 << rs2 _{4:0}
0110011 (51)	010	0000000	R	slt rd, rs1, rs2	set less than	rd = (rs1 < rs2)
0110011 (51)	011	0000000	R	sltu rd, rs1, rs2	set less than unsigned	rd = (rs1 < rs2)
0110011 (51)	100	0000000	R	xor rd, rs1, rs2	xor	rd = rs1 ^ rs2
0110011 (51)	101	0000000	R	srl rd, rs1, rs2	shift right logical	rd = rs1 >> rs2 _{4:0}
0110011 (51)	101	0100000	R	sra rd, rs1, rs2	shift right arithmetic	rd = rs1 >>> rs2 _{4:0}
0110011 (51)	110	0000000	R	or rd, rs1, rs2	or	rd = rs1 rs2
0110011 (51)	111	0000000	R	and rd, rs1, rs2	and	rd = rs1 & rs2

In this type, both the operands are from register file, while the instruction specifies the register names to be used in **rs1** and **rs2**


Top Module:



```
--
23 module top_single_cycleRI(
24     input logic clk,
25     input logic rst,
26     output logic [31:0]alu_OUT
27 );
28
29     logic [31:0]count_pc;
30     logic [31:0]Instruction;
31
32     //control instructions
33     logic regWrite; // control for write register
34     logic alusrc;
35     logic ALUop;
36
37     //source registers values
38     logic [31:0]rs0;// for source registers
39     logic [31:0]rs1;
40
41     // imidiata to mux output
42     logic [31:0]Im_mux;
43
44     //MUX output |
45     logic [31:0]ALu_input2;
46
47     // alu control signal form alucontrol
48     logic [4:0]Alucont;
49
50
```

```
--
51     // program counter
52     PC p1(
53         .clk(clk),
54         .reset(rst),
55         .pc(count_pc)
56     );
57
58     //instruction memory
59     Instruction_memory Iml(
60         .counter(count_pc),
61         .instruction(Instruction)
62     );
63
64     //register
65     Register_file #(.IS_DEPTH(5), .REGF_DEPTH(32),.REGF_WIDTH(32),.Opcode (7)) r1l(
66         .clk(clk),
67         .rst(rst),
68         .regWrite(regWrite),
69         .rs1(Instruction[19:15]),
70         .rs2(Instruction[24:20]),
71         .rd(Instruction[11:7]),
72         .data_wr(alu_OUT),
73         .s1(rs0),
74         .s2(rs1)
75     );
--
```

Top Module:

 

```
// control module instantiation
```

```
Control cl(
  .opcode(Instruction[6:0]),
  .Regwrit(regWrite),
  .alusrc(alusrc),
  .ALUop(ALUop)
);
```

```
// immediate generator
```

```
Imgen iml(
  .inst(Instruction),
  .imm(Im_mux)
);
```

```
// //MUX
// Mux #(.Imlength(32)) m1(
//   .ALU_src(alusrc),
//   .instr(Im_mux),
//   .source_2(rs1),
//   .RS2(ALu_input2)
// );
```

```
assign ALu_input2 = (alusrc)?Im_mux: rs1;
```

```
//Alu control
```

```
ALU_control al(
  .inst(Instruction),
  .Alu_ctrl(Alucont)
);
```

```
//
// assign ALu_input2 = (alusrc)?Im_mux: rs1;
//Alu control
ALU_control al(
  .inst(Instruction),
  .Alu_ctrl(Alucont)
);
// ALU
ALU #(.REGF_WIDTH(32) , .OP_code(5)) alu1(
  .op_code(Alucont),
  .source1(rs0),
  .source2(ALu_input2),
  .out_put(alu_OUT)
);
```

```
endmodule
```


Test bench:

```

2 |
3 | module pc_tb();
4 |
5 |     parameter size = 1024;
6 |     logic clk;
7 |     logic reset;
8 |     logic [size-1:0] pc;
9 |
10 |    // PC instance
11 |    PC #(size) dut (
12 |        .clk(clk),
13 |        .reset(reset),
14 |        .count(pc)
15 |    );
16 |
17 |    // clock generation (10ns period)
18 |    initial begin
19 |        clk = 0;
20 |        forever #5 clk = ~clk;    // toggle every 5ns
21 |    end
22 |
23 |    // stimulus
24 |    initial begin
25 |
26 |        reset = 1;
27 |        #12;           // keep reset high for some cycles
28 |
29 |        reset = 0;     // release reset
30 |        #50;
31 |

```


Instruction Memory:


Project Summary


Schematic


PC.sv


C:/Single_cycle/Single_cycle.srscs/sim_1/new/lmem.mer
























1	00A00293
2	01400313
3	00500393
4	00620433
5	407304B3
6	006257B3
7	007266B3
8	00F36613
9	00836913
10	FFD20713
11	0000006F

10

Simulation Output:

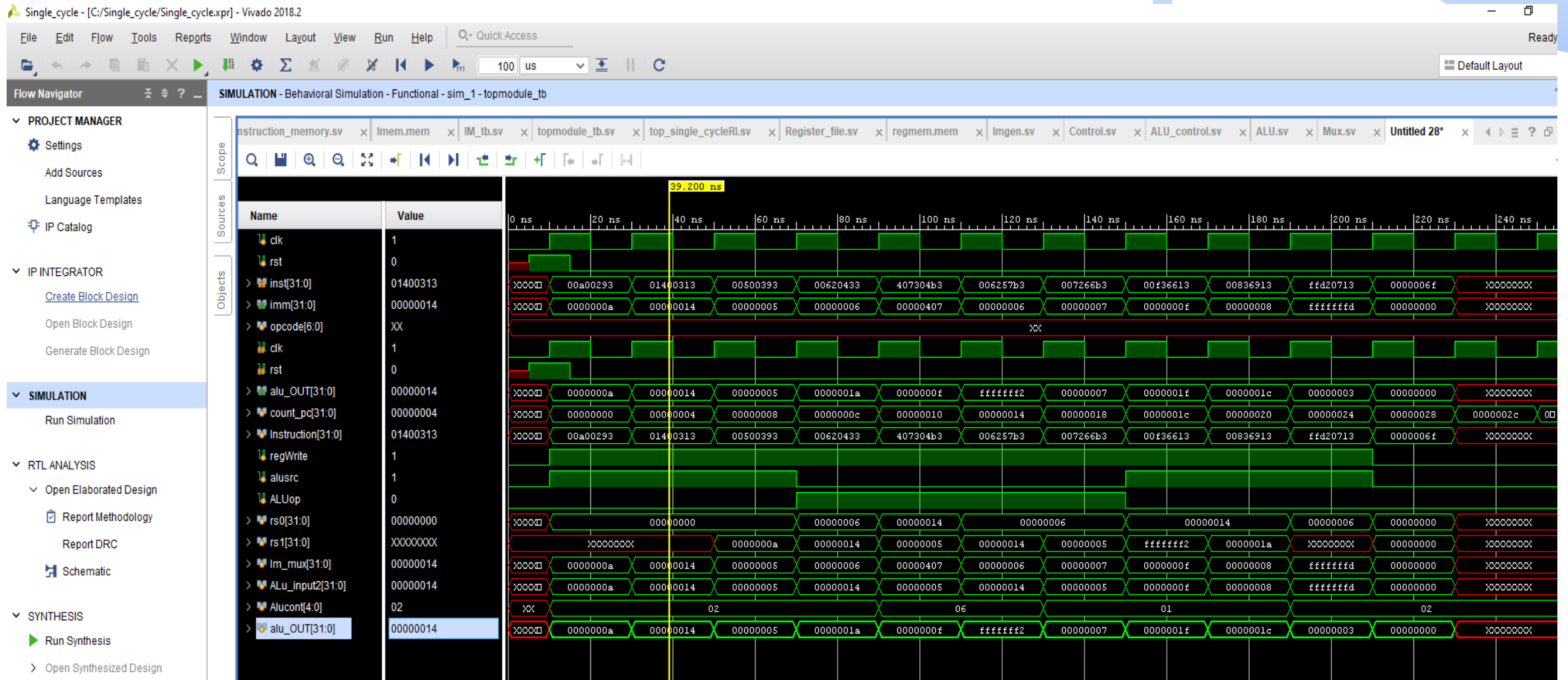

Assembly code:

Code Assembly - Notepad

File Edit Format View Help

```
#Load Values
addi x1 x0 2
addi x2 x0 4
#R-Type Instructions
add x3 x1 x2
sub x4 x2 x1
and x5 x1 x2
or x6 x1 x2
xor x7 x1 x2
sll x8 x1 x2
srli x9 x2 x1
sra x10 x2 x1
#I-Type Instructions
addi x11 x1 3
andi x12 x1 3
ori x13 x1 3
xori x14 x1 3
slli x15 x1 3
srli x16 x2 1
srai x17 x2 1
```

Instruction Memory:


Code Dump.mem - Notepad

File Edit Format View Help



```
0x00200093
0x00400113
0x002081B3
0x40110233
0x0020F2B3
0x0020E333
0x0020C3B3
0x00209433
0x001154B3
0x40115533
0x00308593
0x0030F613
0x0030E693
0x0030C713
0x00309793
0x00115813
0x40115893
```

Simulation Output:

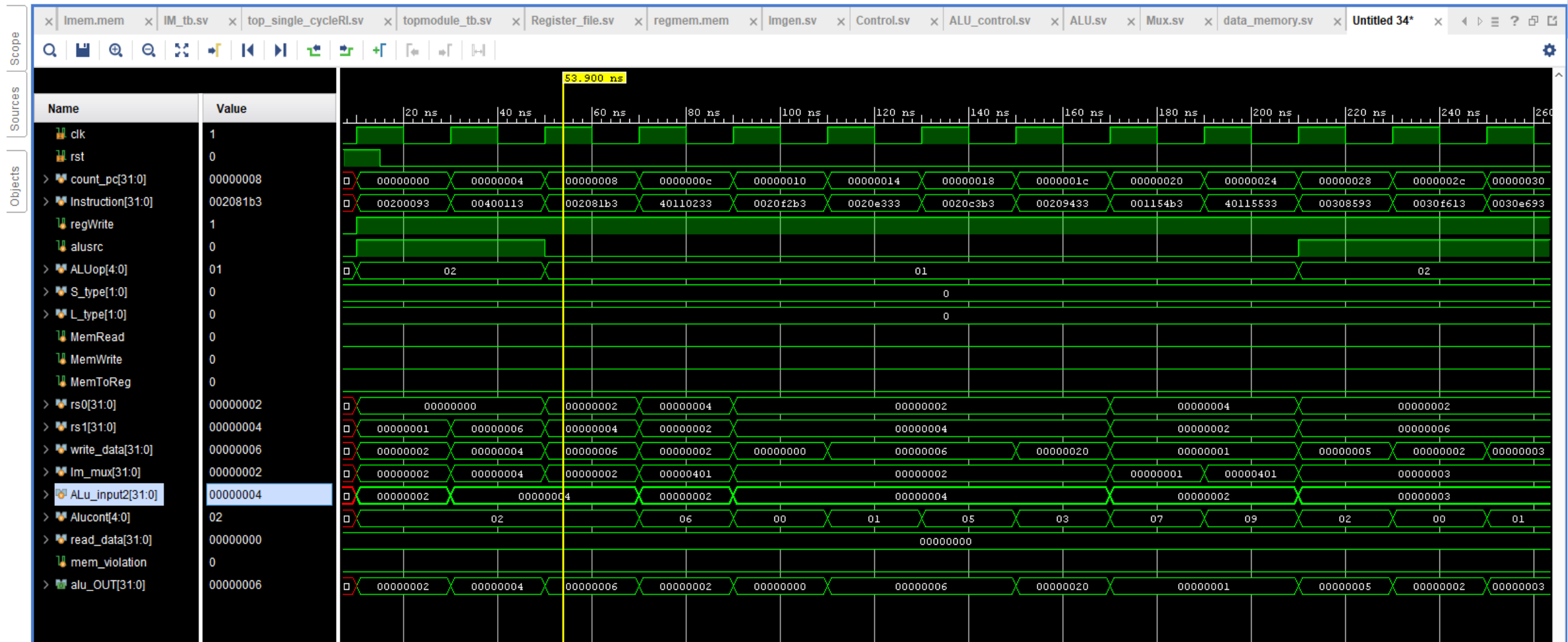SIMULATION - Behavioral Simulation - Functional - sim_1 - topmodule_tb



13 Elaborated Design IR:

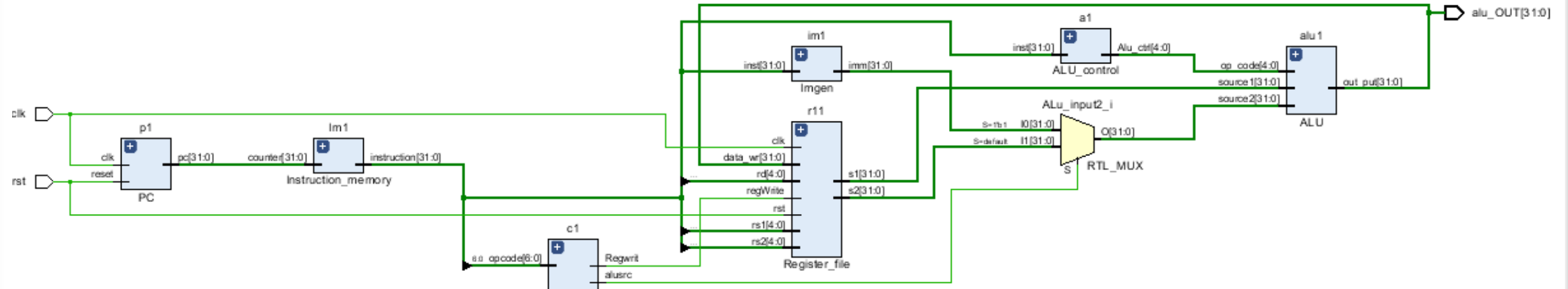 

Summary

It implements a **single-cycle RISC-V datapath** that:

Fetches the instruction from instruction memory using the program counter.

Decodes the instruction to generate control signals.


Reads operands from the register file.

Generates immediate values when needed.

Selects between register operand or immediate for ALU input.

Performs the ALU operation (add, sub, etc.) based on instruction.

Writes back the ALU result into the destination register.

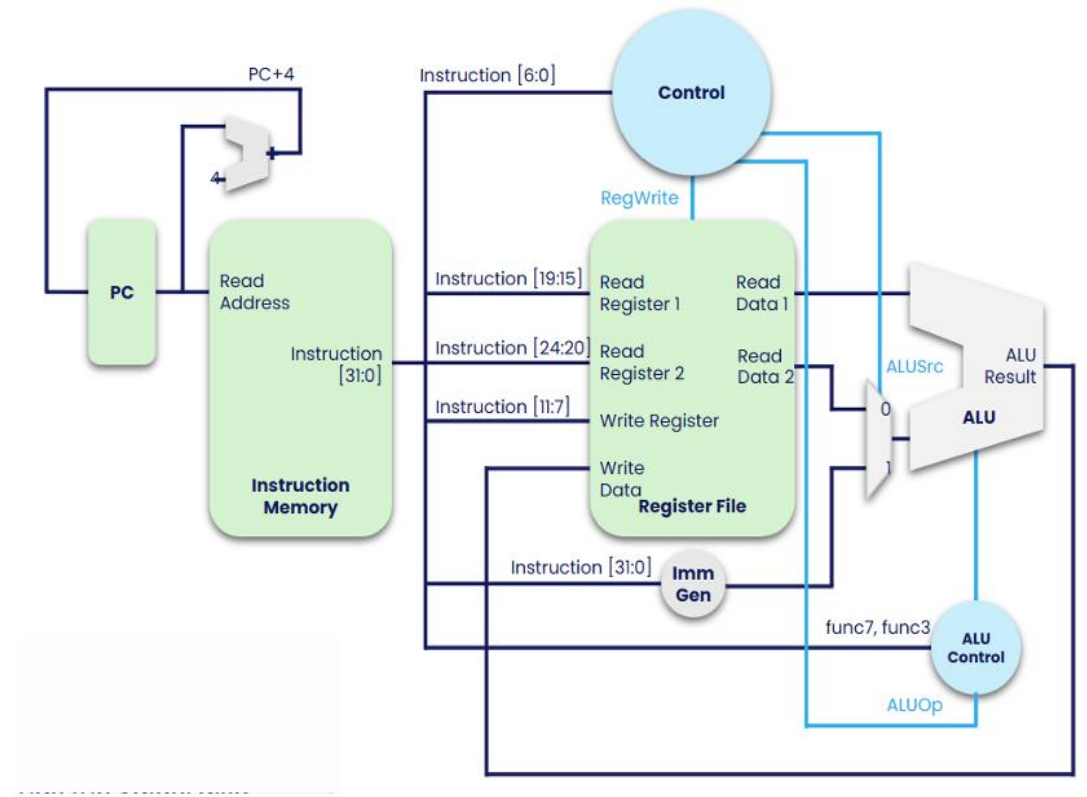


Part 2: Load Store Instructions

Module changes:

Immediate generator :

Control(control signals) :

Data_memory(New ☹):

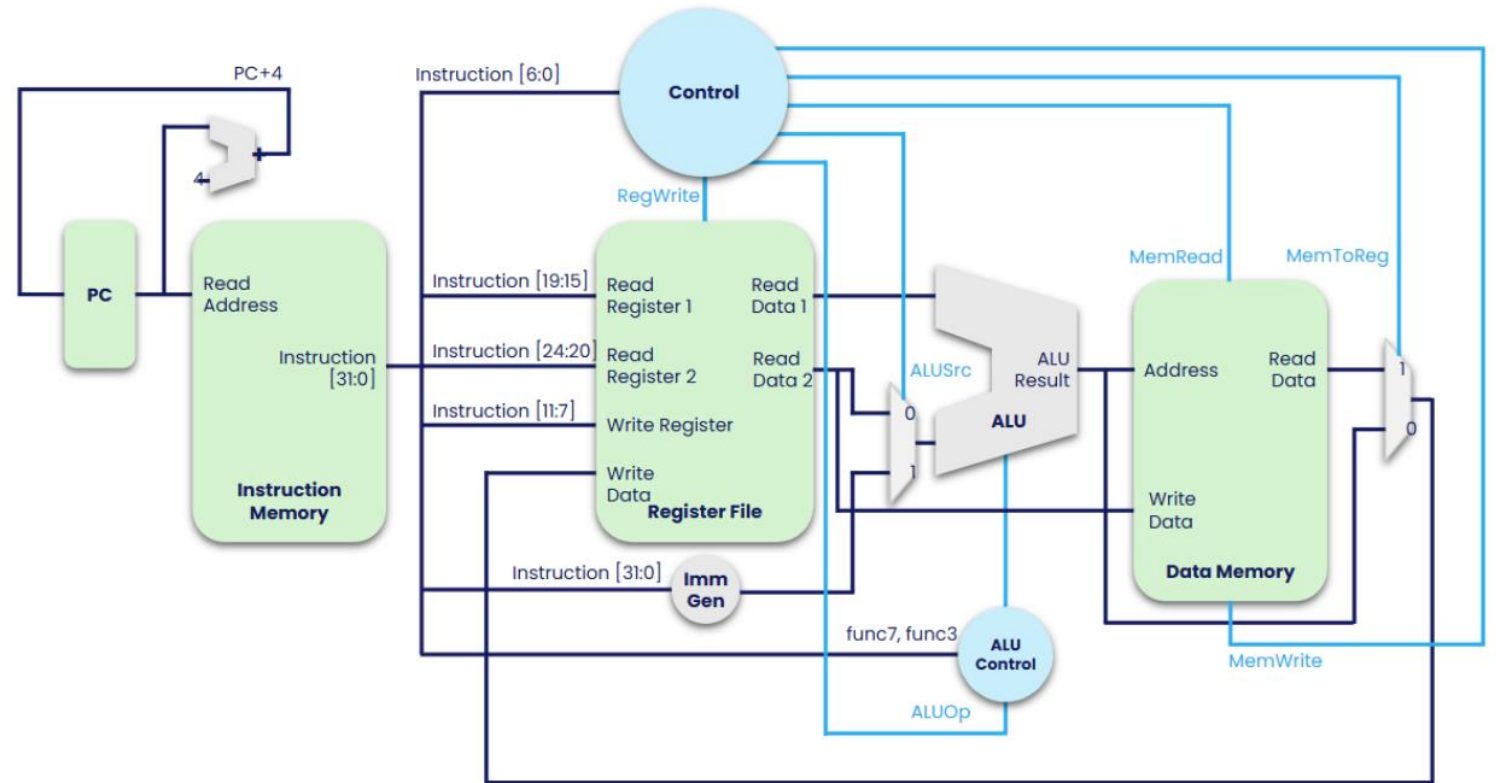

Complete Architecture



```

23 module data_memory(
24     input clk,
25     input logic [31:0]address,
26     input logic [31:0]write_data,
27     input logic MemRead,
28     input logic MemWrite,
29     input logic [1:0] l_type,
30     input logic [1:0] s_type,
31     output logic [31:0]read_data,
32     output logic mem_violation
33 );
34
35     logic [31:0]DATA_MEM[0:256];
36     logic [31:0] word;
37
38     // Default outputs
39     assign word = DATA_MEM[address[9:2]];
40
always_ff @(posedge clk) begin
    if (MemWrite && !mem_violation) begin
        case (s_type)
            2'b00: begin // SB
                case (address[1:0])
                    2'b00: DATA_MEM[address[9:2]][7:0] <= write_data[7:0];
                    2'b01: DATA_MEM[address[9:2]][15:8] <= write_data[7:0];
                    2'b10: DATA_MEM[address[9:2]][23:16] <= write_data[7:0];
                    2'b11: DATA_MEM[address[9:2]][31:24] <= write_data[7:0];
                endcase
            end
            2'b01: begin // SH
                if (address[1]==1'b0)
                    DATA_MEM[address[9:2]][15:0] <= write_data[15:0];
                else
                    DATA_MEM[address[9:2]][31:16] <= write_data[15:0];
                end
            end
            2'b10: begin // SW
                DATA_MEM[address[9:2]] <= write_data;
            end
        endcase
    end
end

```

```

always_comb begin
    mem_violation = 1'b0;
    case (l_type)
        (MemRead || MemWrite) && (l_type==2'b10 || s_type==2'b10):
            mem_violation = (address[1:0] != 2'b00); // word must be aligned
        (MemRead || MemWrite) && (l_type==2'b01 || s_type==2'b01):
            mem_violation = (address[0] != 1'b0); // half must be aligned
        default: ;
    endcase
end

// Read (combinational)
always_comb begin
    read_data = 32'b0;
    if (MemRead && !mem_violation) begin
        case (l_type)
            2'b00: // LB (sign-extend byte)
                read_data = {{24{word[8*address[1:0]+7]}}, word >> (8*address[1:0]) & 8'hFF};
            2'b01: // LH (sign-extend halfword)
                read_data = {{16{word[16*address[1]+15]}}, word >> (16*address[1]) & 16'hFFFF};
            2'b10: // LW (word)
                read_data = word;
            default:
                read_data = 32'b0;
        endcase
    end
end

```


Memory Alignment:

Memory Alignment

To simplify the circuitry, the data memory can only access 32-Bits at a time. Regardless of what the load/store instruction you may have **dataR** and **dataW** will always be 32-bits long. In addition, many RISC-V Memories have a further restriction that data memory can only access addresses that are multiples of 4. RISC-V often mandates that loads/stores happen on aligned addresses, that is

1. **lw/sw** happens at addresses that are multiples of 4.
2. **lh/sh** happens at addresses that are multiples of 2.
3. **lb/sb** can happen at any address.
4. **lhu (Load Halfword Unsigned)**: Loads a 16-bit halfword from memory into a register and zero-extends it to 32 bits.
5. **lbu (Load Byte Unsigned)**: Loads an 8-bit byte from memory into a register and zero-extends it to 32 bits.

Unaligned accesses have undefined behavior. In the case of loads, the half-words/bytes may be selected from the 32-Bit word and Sign/Zero extended based on the instruction. In the case of stores, data smaller than word size may be manipulated to align with the right bytes, and a mask may be applied to avoid unnecessary overwrites (separate read/write bits).

- **Alignment checks (memory violations):**
 - LW/SW → address must be multiple of 4.
 - LH/SH → address must be multiple of 2.
 - LB/SB → no restriction.
- **Selective masking:**
 - For byte and halfword stores, only update the required bytes inside the word.
 - For loads, select the right portion of the word and apply **sign-extension / zero-extension**.

Instruction for load store:

Stores (S-Type)

The store instructions are encoded in a special instruction type known as the S-Type (bear in mind that S does not stand for Special). The encoding of S-Type is as follows:



It is slightly different from the I-Type. The destination register operand is replaced with the immediate value while the source operand (rs2) is brought back, leading to breaking down of immediate into two fields. Breaking down ensures uniformity in the fields (rs1, rs2, rd, etc.).

op	funct3	funct7	Type	Instruction	Description	Operation
0100011 (35)	000	–	S	sb rs2, imm(rs1)	store byte	[Address] _{7:0} = rs2 _{7:0}
0100011 (35)	001	–	S	sh rs2, imm(rs1)	store half	[Address] _{15:0} = rs2 _{15:0}
0100011 (35)	010	–	S	sw rs2, imm(rs1)	store word	[Address] _{31:0} = rs2

```

7'b0100011: begin    // Store
    Regwrit = 0;
    alusrc   = 1;
    ALUOp    = 5'b00100;
    MemWrite = 1;
    case (funct3)
        3'b000: S_type = 2'b00; // SB
        3'b001: S_type = 2'b01; // SH
        3'b010: S_type = 2'b10; // SW
        default: S_type = 2'b00;
    endcase
end

```

Control signals for Store

Instruction for load store:

Loads (I-Type)

The load instructions are encoded as I-Type Instructions.



A list of load instructions is given in the table below.

op	funct3	funct7	Type	Instruction	Description	Operation
0000011 (3)	000	-	I	lb rd, imm(rs1)	load byte	rd = SignExt([Address] _{7:0})
0000011 (3)	001	-	I	lh rd, imm(rs1)	load half	rd = SignExt([Address] _{15:0})
0000011 (3)	010	-	I	lw rd, imm(rs1)	load word	rd = [Address] _{31:0}
0000011 (3)	100	-	I	lbu rd, imm(rs1)	load byte unsigned	rd = ZeroExt([Address] _{7:0})
0000011 (3)	101	-	I	lhu rd, imm(rs1)	load half unsigned	rd = ZeroExt([Address] _{15:0})

The load instructions function in a similar way to add instructions, with immediate operands. Address is computed inside the ALU and propagated to the data memory to index the required data from memory array.

```

7'b0000011: begin // Load
    Regwrit = 1;
    alusrc = 1;
    ALUop = 5'b00011;
    MemRead = 1;
    MemToReg = 1;
    case(func3)
        3'b000: L_type = 2'b00 ;//lb
        3'b001: L_type = 2'b00 ;//lh
        3'b010: L_type = 2'b00 ;//lw
        default: L_type = 2'b00 ;
    endcase
end

```

Control signals for Load

20 Top module changes:

```
// Data memory
```


```
data_memory dl(  
    .clk(clk),  
    .address(alu_OUT),  
    .write_data(rs1),  
    .MemRead(MemRead),  
    .MemWrite(MemWrite),  
    .l_type(L_type),  
    .s_type(S_type),  
    .read_data(read_data),  
    .mem_violation(mem_violation)  
);
```

```
//mux to control storage or just output
```


```
assign write_data = (MemToReg)? read_data: alu_OUT ;
```

```
// control module instantiation
```

 
```
Control cl(  
    .opcode(Instruction[6:0]),  
    .func3(Instruction[14:12]),  
    .MemRead(MemRead),  
    .MemWrite(MemWrite),  
    .Regwrit(regWrite),  
    .MemToReg(MemToReg),  
    .alusrc(alusrc),  
    .ALUop(ALUop),  
    .L_type(L_type),  
    .S_type(S_type)  
);
```



Elaborated Design/ Schematic:

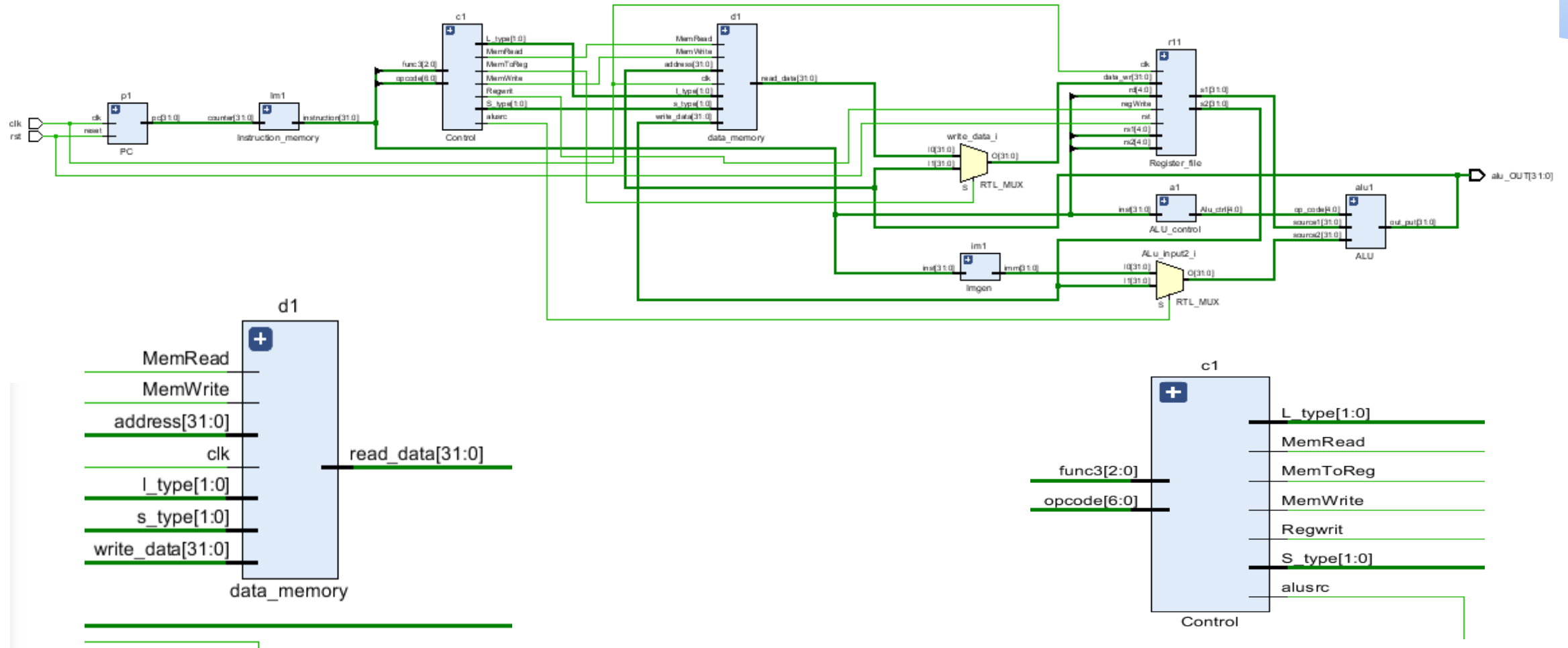

Assembly code:

 *Untitled - Notepad
File Edit Format View Help

Initialize registers
addi x1, x0, 10 # 0x00A00093
addi x2, x0, 20 # 0x01400113
addi x3, x0, -5 # 0xFFB00193



R-type arithmetic
add x4, x1, x2 # 0x002082B3
sub x5, x2, x1 # 0x40110133

Store to memory
sw x4, 0(x0) # 0x00402023
sw x5, 4(x0) # 0x00502223
sb x1, 8(x0) # 0x00104423
sh x2, 12(x0) # 0x00204623

Load from memory
lw x6, 0(x0) # 0x00002303
lh x7, 12(x0) # 0x00C03483
lb x8, 8(x0) # 0x00804403

Logical operations
xor x9, x6, x7 # 0x007343B3
and x10, x6, x7 # 0x00737433
or x11, x6, x7 # 0x007364B3
xori x12, x6, 15 # 0x00F34613
andi x13, x7, 15 # 0x00F4F693
ori x14, x8, 15 # 0x00F46513

Simulation:

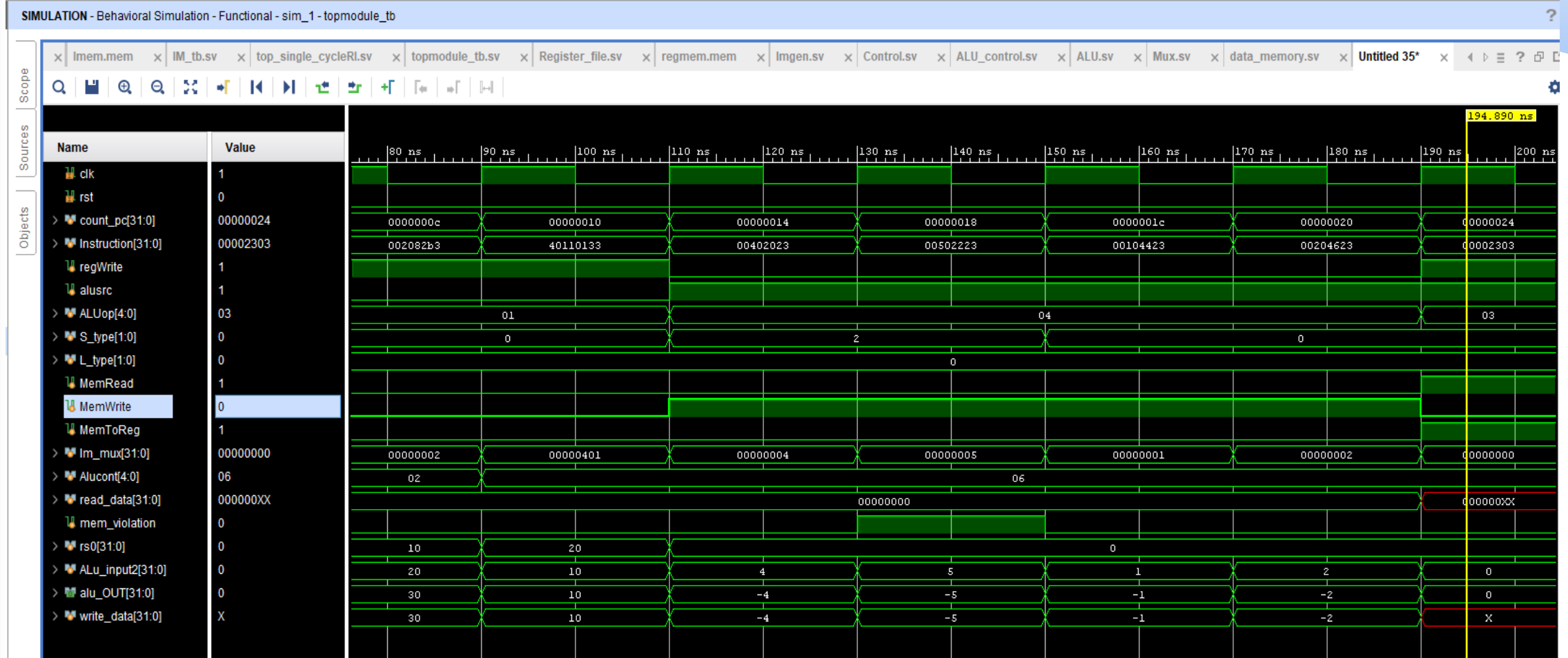 

Part 3: Jumps

Jumps

There are two jump instructions namely

1. jalr (I-Type)
2. jal (J-Type)



The encoding of J-Type is given in the figure below



A list of jump instructions is provided in the table below

op	funct3	funct7	Type	Instruction	Description	Operation
1100111 (103)	000	-	I	jalr rd, rs1, imm	jump and link register	PC = rs1 + SignExt(imm), rd = PC + 4
1101111 (111)	-	-	J	jal rd, label	jump and link	PC = JTA, rd = PC + 4

The **jal** instruction jumps to the address specified in the immediate field, while the **jalr** uses the addresses stored in **rs1** along with immediate values to make longer jumps.

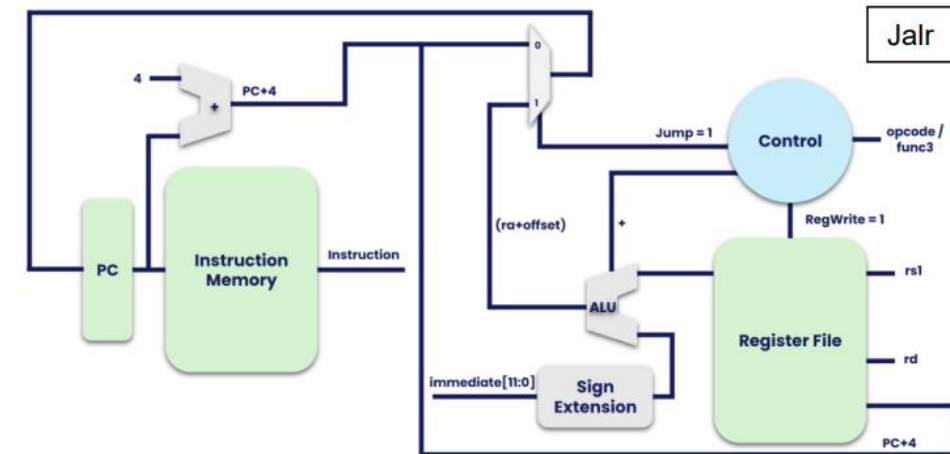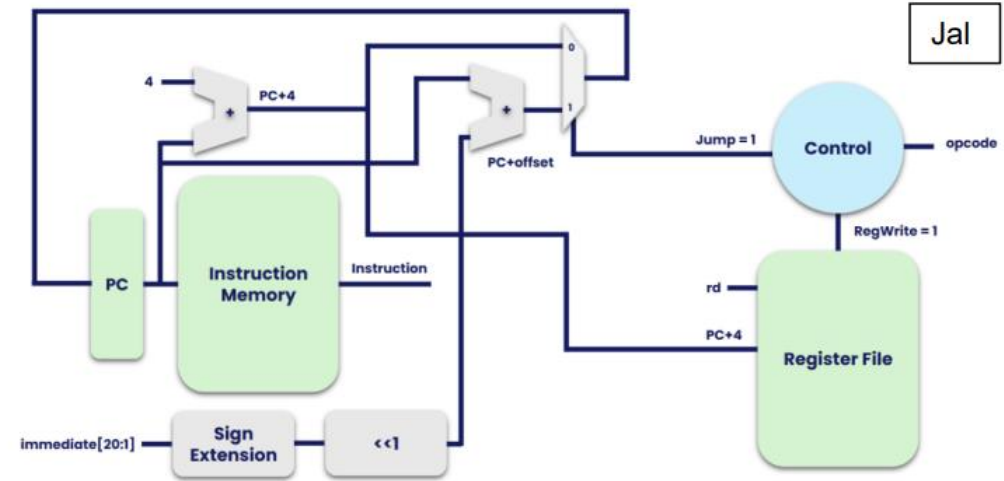

Part 3: Jumps

```
// Data memory
```

```
data_memory dl(
    .clk(clk),
    .address(alu_OUT),
    .write_data(rsl),
    .MemRead(MemRead),
    .MemWrite(MemWrite),
    .l_type(L_type),
    .s_type(S_type),
    .read_data(read_data),
    .mem_violation(mem_violation)
);
```

```
//mux to control storage or just output
```

```
assign write_data = (MemToReg)? read_data: alu_OUT ;
```

```
assign branch_target = count_pc + Im_mux;
```

```
assign PC_Next = (jump)? branch_target: ((branch && zero)? branch_target: count_pc + 4);
```


```

7'b0100011: begin // Store
    imm = {{20{inst[31]}}, inst[31:25], inst[11:7]};
end
7'b1100111: begin
    imm = {{20{inst[31]}}, inst[31:20]}; // jalr
end
7'b1101111: begin
    imm = {{12{inst[31]}}, inst[19:12], inst[20], inst[30:21], 1'b0}; // jal
end

default: begin
    imm = {{20{inst[31]}}, inst[31:20]};
end
endcase
end

```

Assembly code:


 *Untitled - Notepad
File Edit Format View Help
Initialize registers
addi x1, x0, 10 # 0x00A00093
addi x2, x0, 20 # 0x01400113
addi x3, x0, -5 # 0xFFB00193

R-type arithmetic
add x4, x1, x2 # 0x002082B3
sub x5, x2, x1 # 0x40110133

Store to memory
sw x4, 0(x0) # 0x00402023
sw x5, 4(x0) # 0x00502223
sb x1, 8(x0) # 0x00104423
sh x2, 12(x0) # 0x00204623

Load from memory
lw x6, 0(x0) # 0x00002303
lh x7, 12(x0) # 0x00C03483
lb x8, 8(x0) # 0x00804403

Logical operations
xor x9, x6, x7 # 0x007343B3
and x10, x6, x7 # 0x00737433
or x11, x6, x7 # 0x007364B3
xori x12, x6, 15 # 0x00F34613
andi x13, x7, 15 # 0x00F4F693
ori x14, x8, 15 # 0x00F46513

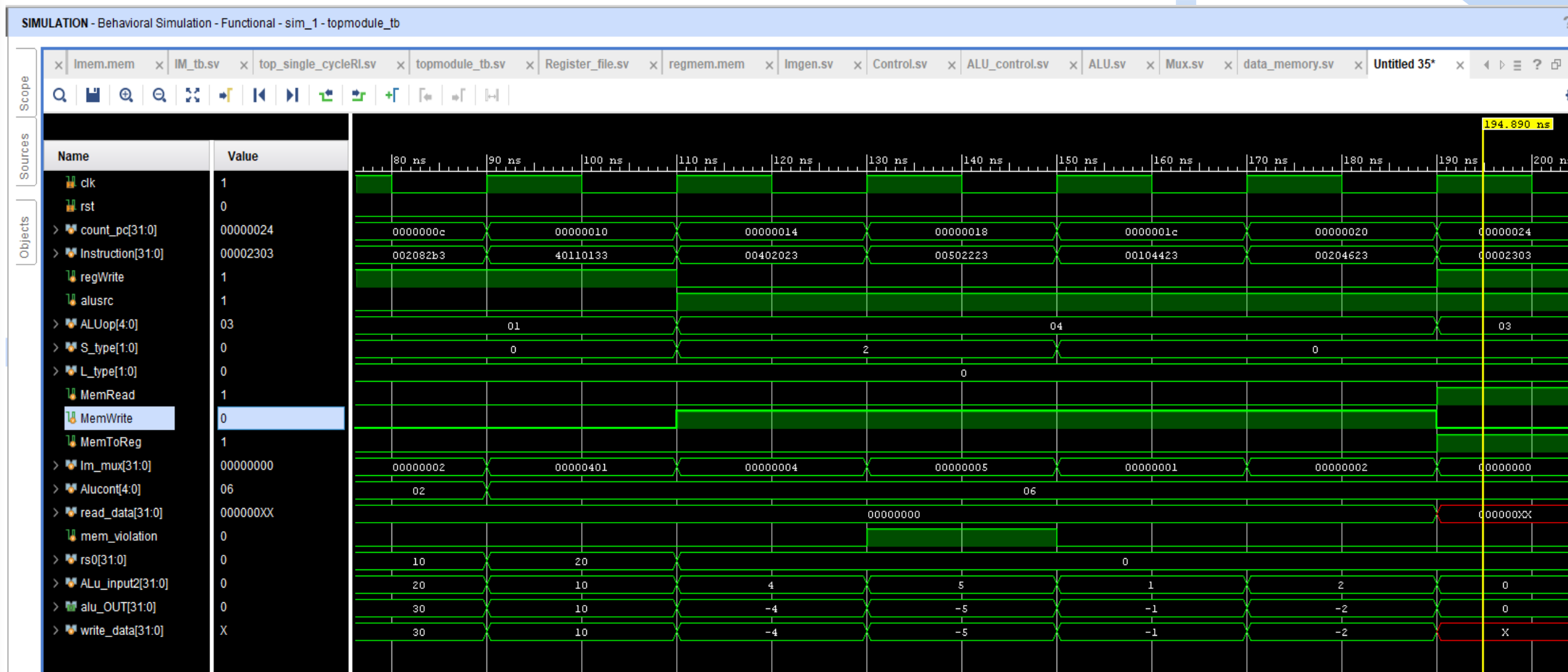

Part 4: Branch and LUI and AUIPC

Branches


There are several types of branch instructions having B-Type Encoding and listed in the table below

imm _{12,10:5}	rs2	rs1	funct3	imm _{4:1,11}	op	B-Type
------------------------	-----	-----	--------	-----------------------	----	--------


op	funct3	funct7	Type	Instruction	Description	Operation
1100011 (99)	000	-	B	beq rs1, rs2, label	branch if =	if (rs1 == rs2) PC = BTA
1100011 (99)	001	-	B	bne rs1, rs2, label	branch if ≠	if (rs1 ≠ rs2) PC = BTA
1100011 (99)	100	-	B	blt rs1, rs2, label	branch if <	if (rs1 < rs2) PC = BTA
1100011 (99)	101	-	B	bge rs1, rs2, label	branch if ≥	if (rs1 ≥ rs2) PC = BTA
1100011 (99)	110	-	B	bltu rs1, rs2, label	branch if < unsigned	if (rs1 < rs2) PC = BTA
1100011 (99)	111	-	B	bgeu rs1, rs2, label	branch if ≥ unsigned	if (rs1 ≥ rs2) PC = BTA

When the branch condition becomes true the processor jumps to the label listed in the instruction. Essentially, label is encoded as an immediate value that specifies the offset from current value of program counter. i.e. $PC = PC + \text{Offset (Label)}$.

 It might seem evident, but for sake of clarity we explain that arithmetic logic unit (ALU) is busy computing program counter address, and we need to we will use ALU for comparing the branch conditions.



Data path:

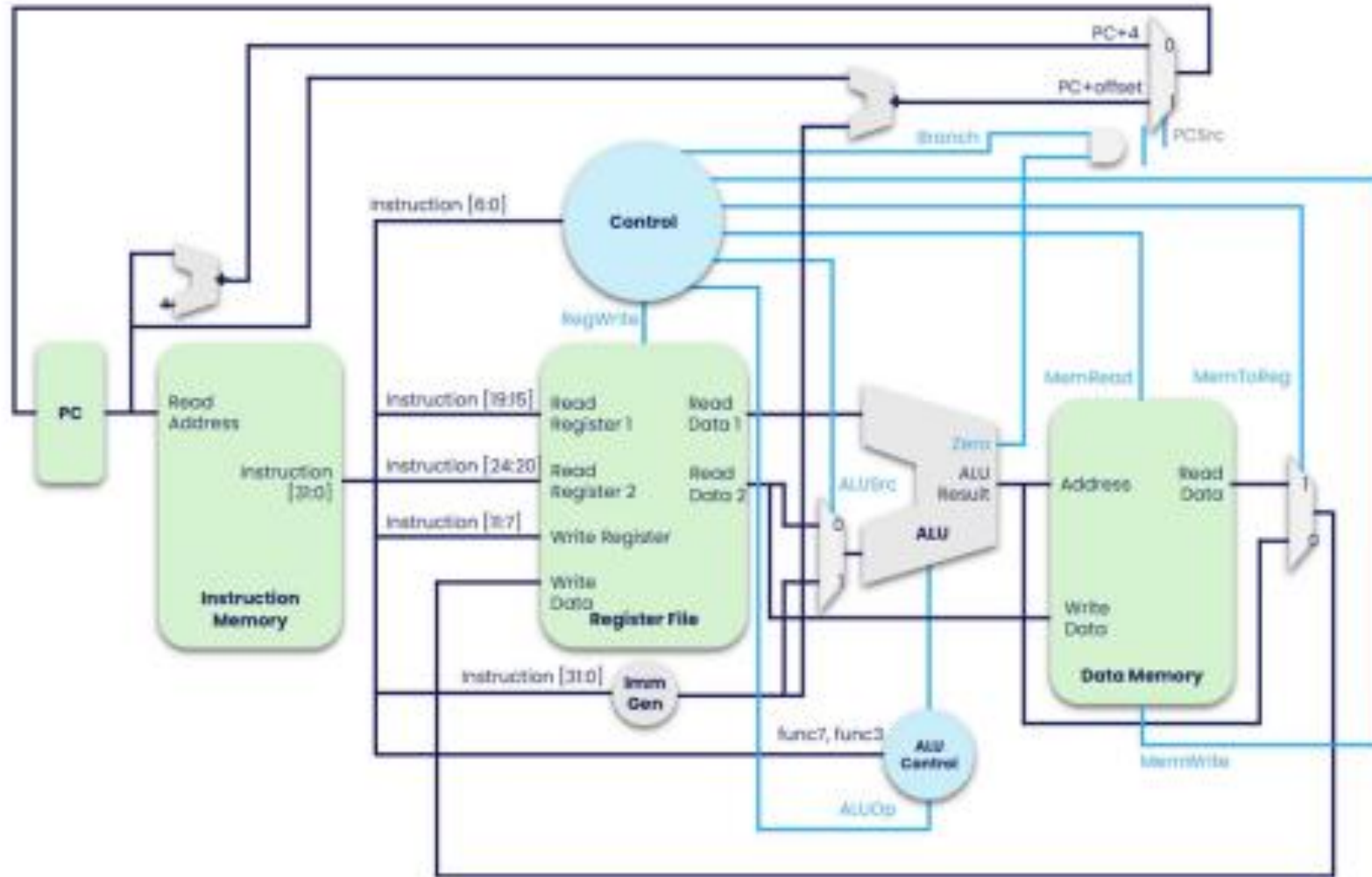

Upper Immediate:



Upper Immediate (U-Type)

The next goal is to extend the design to include upper immediate instructions, encoded as U-Type and listed in the table below.

imm _{31:12}				rd	op	U-Type
op	funct3	funct7	Type	Instruction	Description	Operation
0110111 (55)	-	-	U	lui rd, upimm	load upper immediate	rd = {upimm, 12'b0}
0010111 (23)	-	-	U	auipc rd, upimm	add upper immediate to PC	rd = {upimm, 12'b0} + PC


```

7'b1100011: begin // Branch (B-type)
    imm = {{20{inst[31]}}, inst[7], inst[30:25], inst[11:8], 1'b0};
end
7'b0110111: begin // LUI (U-type)
    imm = {inst[31:12], 12'b0};
end
7'b0010111: begin // AUIPC (U-type)
    imm = {inst[31:12], 12'b0};


```

Control Path:


```
7'b110011: begin // Branch
    Regwrit = 0;
    alusrc = 1;
    ALUop = 5'b01011;
    Branch = 1;
    MemRead = 0;
    MemWrite = 0;
end
7'b0110111: begin // LUI
    Regwrit = 1;
    alusrc = 1;
    MemRead = 0;
    MemWrite = 0;
    Branch = 0 ;
    ALUop = 5'b01010;
end
7'b0110111: begin // AUIPC
    Regwrit = 1;
    alusrc = 1;
    MemRead = 0;
    MemWrite = 0;
    Branch = 0 ;
    ALUop = 5'b00010;
    AUI_pc = 1;
end
```

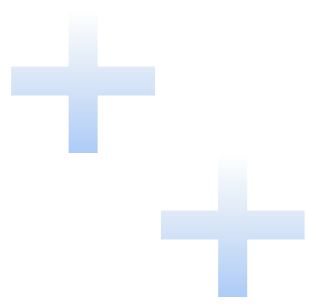

Here various flags are included as controls for the data path, these control flags control the flow, and help other modules and logics to Act properly.




Branch condition Logic:

 

```
// Branch condition logic
always_comb begin
    branch_taken = 1'b0; // default
    if (Instruction[6:0] == 7'b1100011) begin // only BRANCH type
        case (Instruction[14:12]) // funct3
            3'b000: branch_taken = (rs0 == rs1);
            3'b001: branch_taken = (rs0 != rs1);
            3'b100: branch_taken = ($signed(rs0) < $signed(rs1));
            3'b101: branch_taken = ($signed(rs0) >= $signed(rs1));
            3'b110: branch_taken = (rs0 < rs1);
            3'b111: branch_taken = (rs0 >= rs1);
            default: branch_taken = 1'b0;
        endcase
    end
end
```

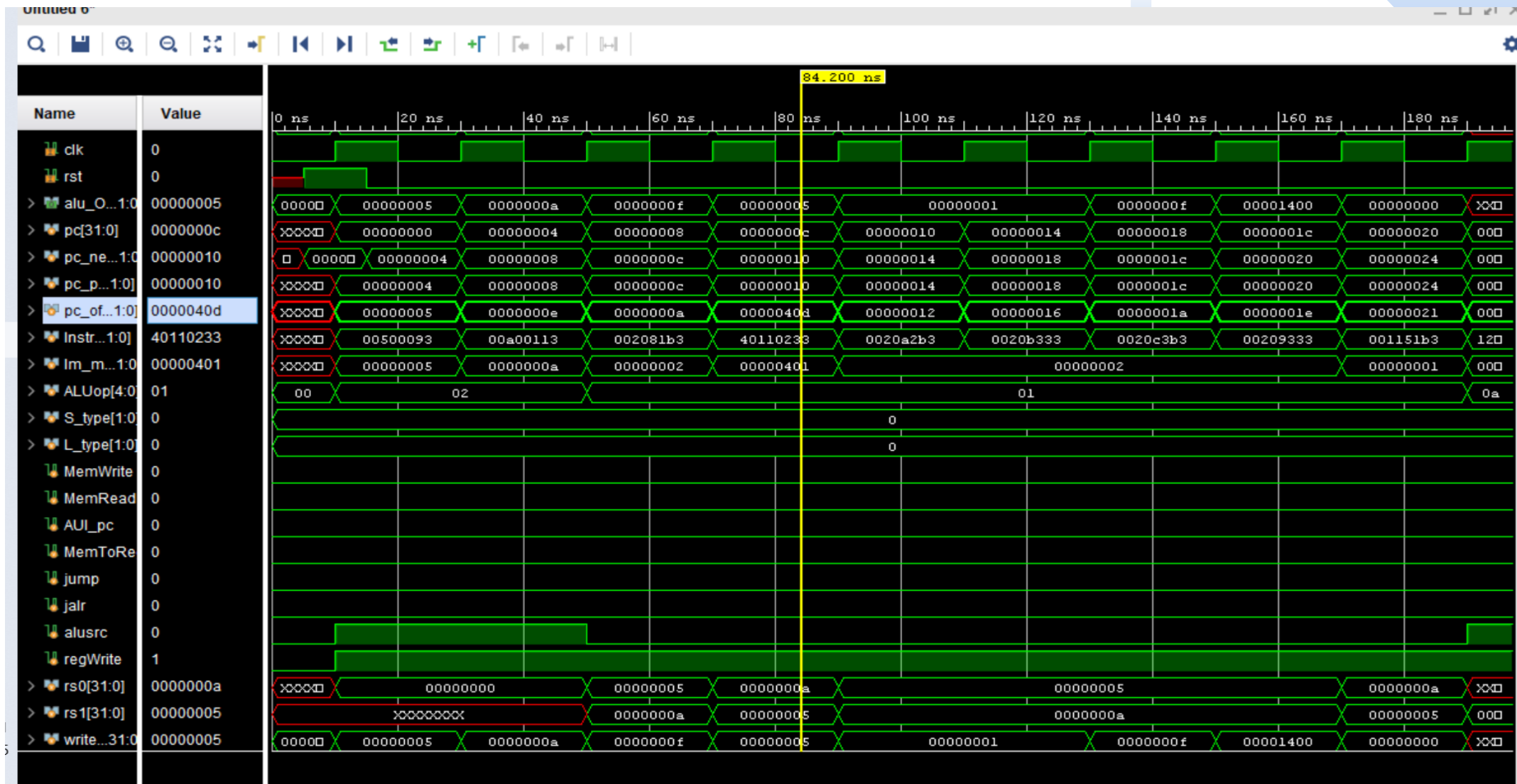In this logic control block we handled different types of branch conditions.



Self evaluation:




```


-
# Test the RISC-V processor:
#   add, sub, and, or, slt, addi, lw, sw, beq, jal
# If successful, it should write the value 25 to address 100
#
# RISC-V Assembly      Description      Address  Machine Code
main:  addi x2, x0, 5      # x2 = 5          0        00500113
      addi x3, x0, 12     # x3 = 12         4        00C00193
      addi x7, x3, -9     # x7 = (12 - 9) = 3  8        FF718393
      or   x4, x7, x2     # x4 = (3 OR 5) = 7  C        0023E233
      and  x5, x3, x4     # x5 = (12 AND 7) = 4 10       0041F2B3
      add  x5, x5, x4     # x5 = 4 + 7 = 11   14       004282B3
      beq  x5, x7, end     # shouldn't be taken 18       02728863
      slt  x4, x3, x4     # x4 = (12 < 7) = 0  1C       0041A233
      beq  x4, x0, around  # should be taken   20       00020463
      addi x5, x0, 0      # shouldn't execute  24       00000293
around: slt  x4, x7, x2    # x4 = (3 < 5) = 1   28       0023A233
      add  x7, x4, x5     # x7 = (1 + 11) = 12 2C       005203B3
      sub  x7, x7, x2     # x7 = (12 - 5) = 7  30       402383B3
      sw   x7, 84(x3)     # [96] = 7          34       0471AA23
      lw   x2, 96(x0)     # x2 = [96] = 7      38       06002103
      add  x9, x2, x5     # x9 = (7 + 11) = 18 3C       005104B3
      jal  x3, end        # jump to end, x3 = 0x44 40      008001EF
      addi x2, x0, 1      # shouldn't execute  44       00100113
end:    add  x2, x2, x9    # x2 = (7 + 18) = 25 48       00910133
      sw   x2, 0x20(x3)   # [100] = 25        4C       0221A023
done:   beq  x2, x2, done  # infinite loop      50       00210063

```

Simulation results:

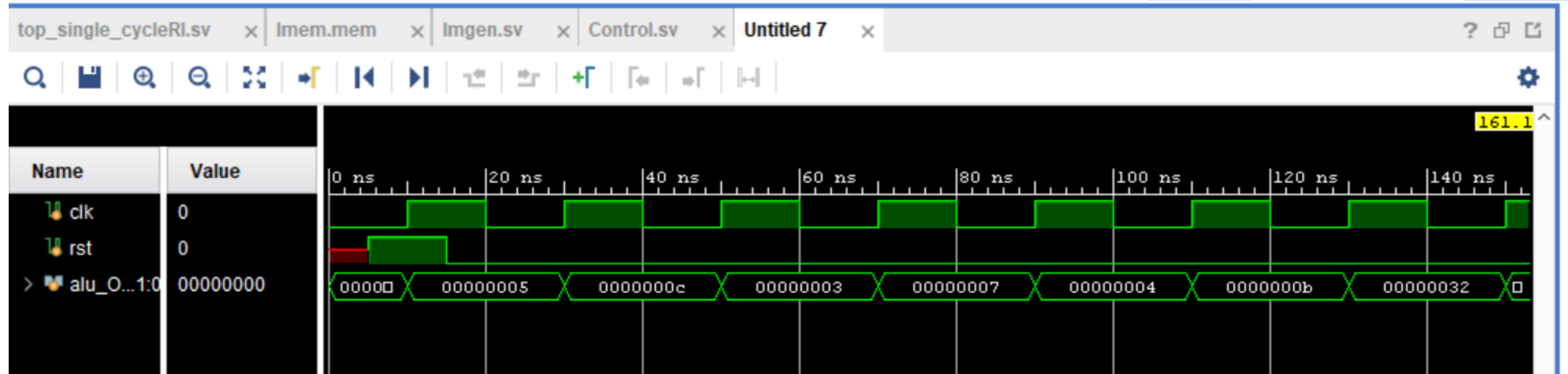

Outputs:

 


```
# run 1000ns
PC=xxxxxxxx Instr=xxxxxxxx Branch=0 Taken=0 imm=xxxxxxxx rs0=xxxxxxxx rs1=xxxxxxxx
PC=00000000 Instr=00500113 Branch=0 Taken=0 imm=00000005 rs0=00000000 rs1=xxxxxxxx
PC=00000004 Instr=00c00193 Branch=0 Taken=0 imm=0000000c rs0=00000000 rs1=xxxxxxxx
PC=00000008 Instr=ff718393 Branch=0 Taken=0 imm=ffffffff7 rs0=0000000c rs1=xxxxxxxx
PC=0000000c Instr=0023e233 Branch=0 Taken=0 imm=00000002 rs0=00000003 rs1=00000005
PC=00000010 Instr=0041f2b3 Branch=0 Taken=0 imm=00000004 rs0=0000000c rs1=00000007
PC=00000014 Instr=004282b3 Branch=0 Taken=0 imm=00000004 rs0=00000004 rs1=00000007
PC=00000018 Instr=02728863 Branch=1 Taken=0 imm=00000027 rs0=0000000b rs1=00000003
PC=0000001c Instr=0041a233 Branch=0 Taken=0 imm=00000004 rs0=0000000c rs1=00000007
PC=00000020 Instr=00020463 Branch=1 Taken=1 imm=00000000 rs0=00000000 rs1=00000000
PC=00000024 Instr=00000000 Branch=0 Taken=0 imm=00000000 rs0=00000000 rs1=00000000
```

Schematics:



Brach_taken logic schematics

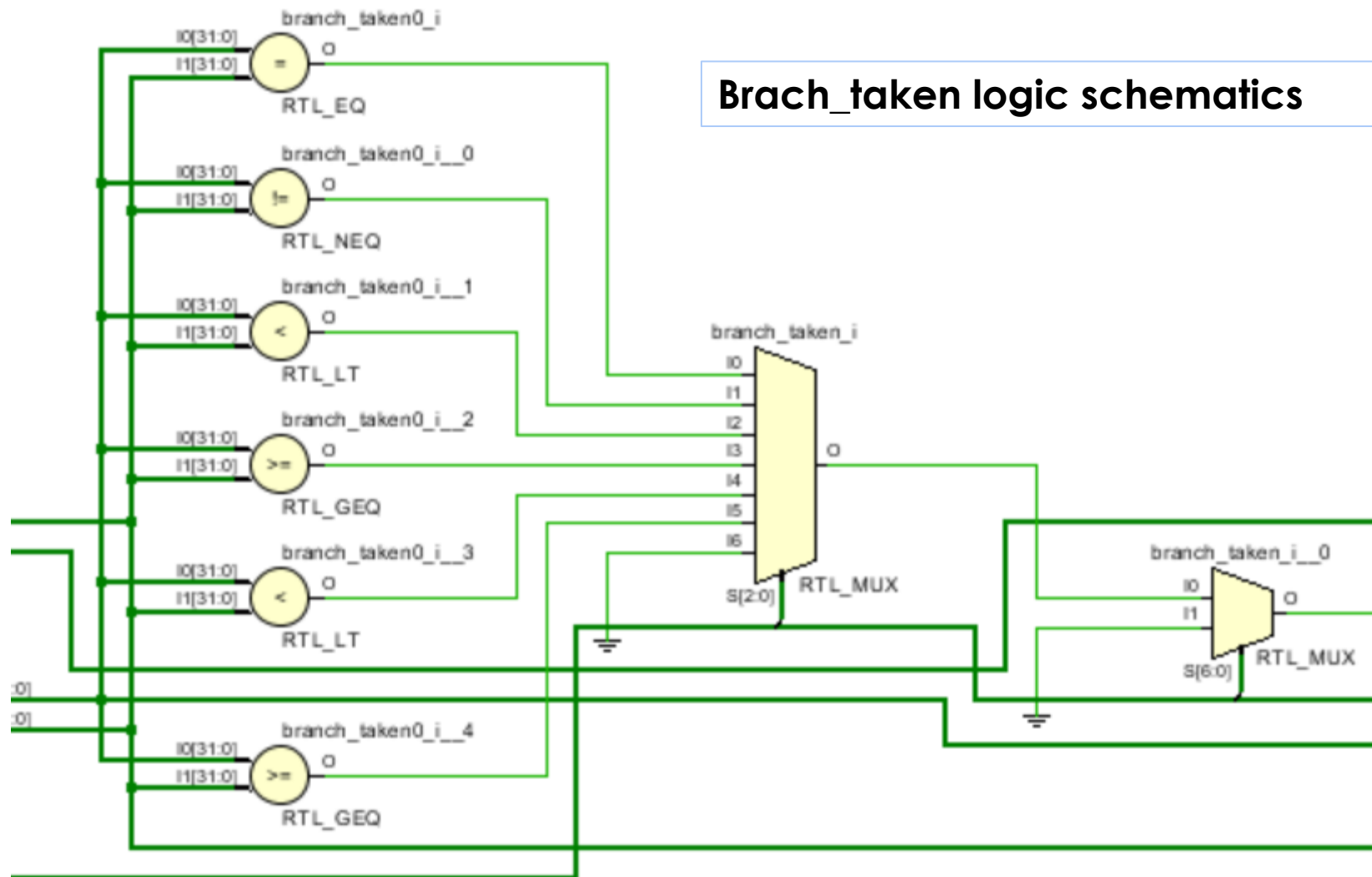


PC logic:


```

always_comb begin
    if (rst) begin
        pc_next = 32'b0;
    end
    else if (jump) begin
        pc_next = pc + Im_mux;    // JAL uses
    end
    else if (jalr) begin
        pc_next = (rs1 + Im_mux) & ~32'b1;
    end
    else if (Branch && branch_taken) begin
        pc_next = pc + Im_mux;    // Branch o
    end
    else begin
        pc_next = pc + 32'd4; // default seq
    end
end
end


```

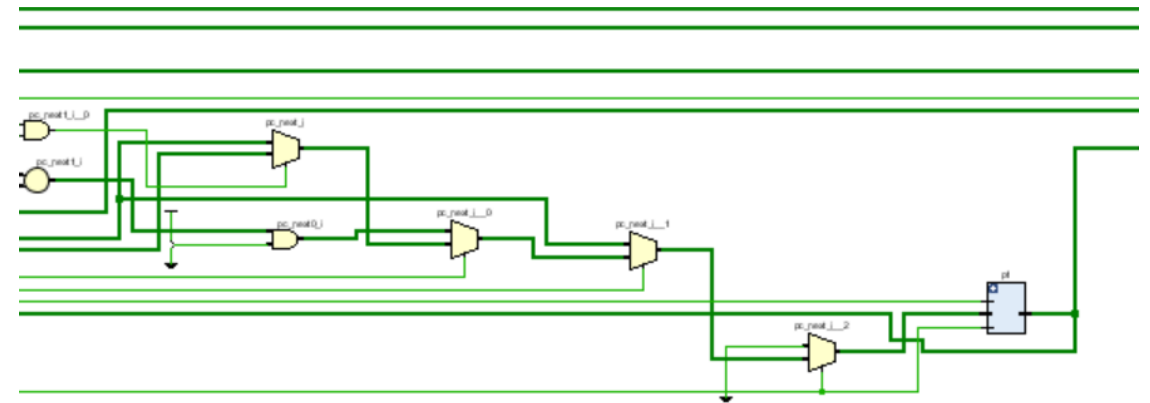

Simulations Output:

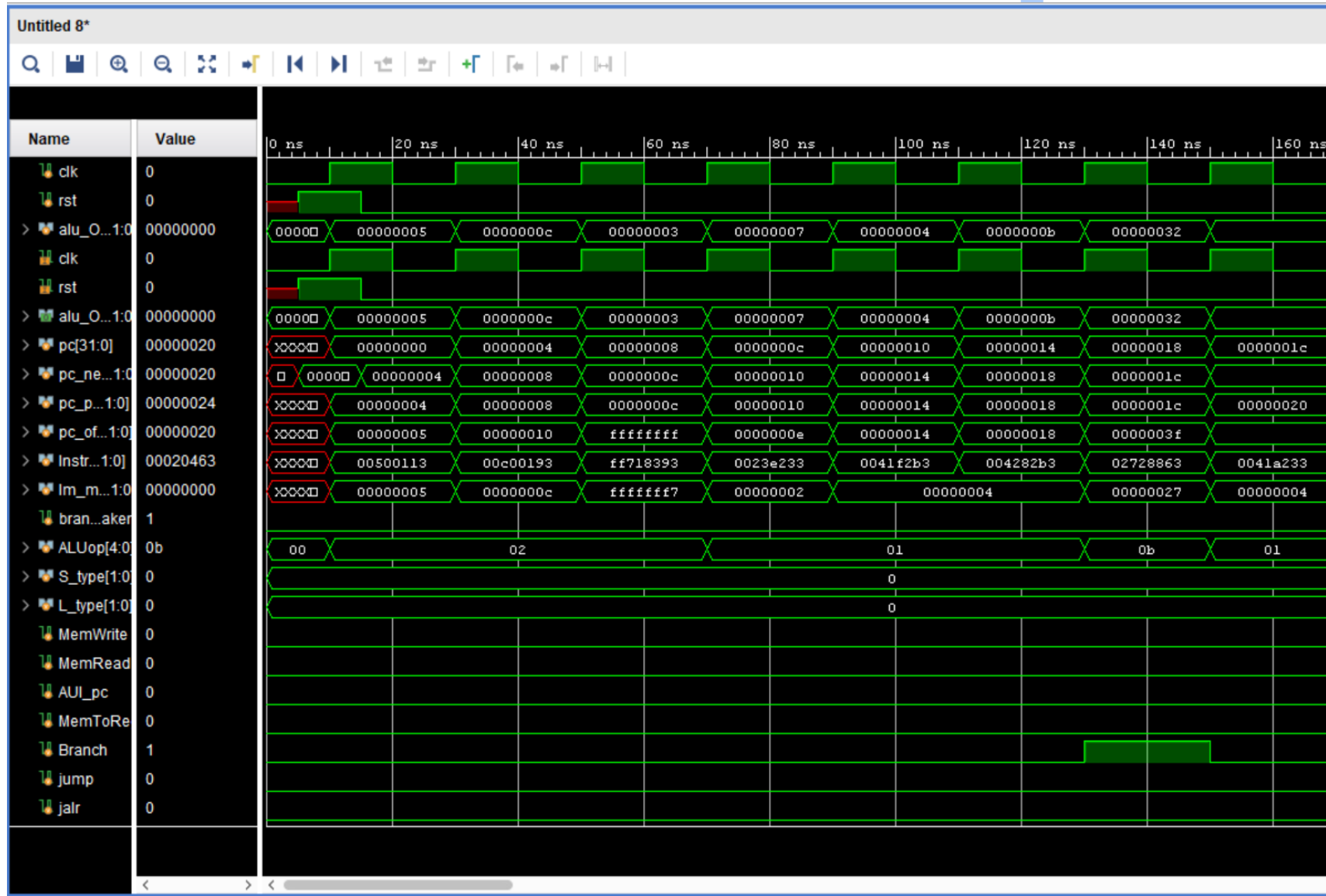


Conclusions:

 

- Implemented a single-cycle RISC-V processor in SystemVerilog
- Supports arithmetic, logical, load/store, and jump instructions
- Verified instruction execution through test programs (hex codes)
- Correct working of PC, ALU, register file, immediate generator, and memory
- Learned integration of datapath and control logic
- Single-cycle design works but has long critical path (low efficiency)
- Future scope: Multi-cycle or pipelined RISC-V processor for better performance

Thank you

 

Muhammad Farhan Shah

farhaanshah336@gmail.com